
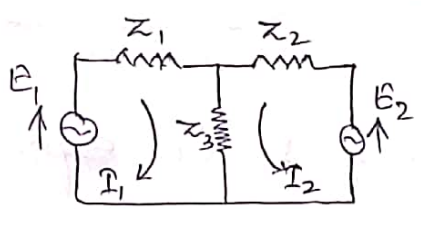


Superposition theorem:

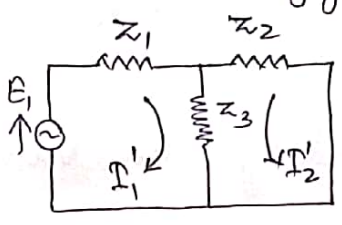
In any linear network containing impedances and energy sources, the current flowing in any element is the vector sum of the currents that are separately caused to flow in that element by each energy source.



fig(1)(a) Two mesh network



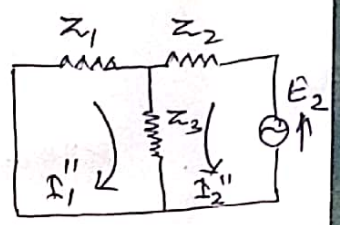fig(1)(b) Two mesh network when E2 is removed.



fig(1)(c) Two mesh network when E1 is removed.

Consider the two voltage sources  $E_1$  and  $E_2$  are three impedances  $Z_1, Z_2$  and  $Z_3$  as shown in figure. Let  $I_1$  and  $I_2$  be the two mesh currents then the mesh equation can be written as,

$$E_1 = (Z_1 + Z_3) I_1 + Z_3 I_2 \quad \text{--- (1)}$$

$$E_2 = (Z_3 I_1) + (Z_2 + Z_3) \cdot I_2 \quad \text{--- (2)}$$

From equation (2) we get,

$$E_2 - (Z_2 + Z_3) \cdot I_2 = Z_3 I_1$$

$$\Rightarrow I_1 = \frac{E_2}{Z_3} - \frac{(Z_2 + Z_3) \cdot I_2}{Z_3}$$

Putting the value of  $I_1$  in equation (1) we get,

$$E_1 = (Z_1 + Z_3) \left[ \frac{E_2}{Z_3} - \frac{(Z_2 + Z_3) I_2}{Z_3} \right] + Z_3 I_2$$

$$\Rightarrow E_1 = \frac{(Z_1 + Z_3) E_2}{Z_3} - \frac{(Z_1 + Z_3)(Z_2 + Z_3) I_2}{Z_3} + Z_3 I_2$$



$$E_1 = \frac{(\alpha_1 + \alpha_3) E_2}{\alpha_3} - \frac{(\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3) I_2}{\alpha_3} \quad (2)$$

$$I_2 = - \frac{E_1 \alpha_3}{\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3} + \frac{(\alpha_1 + \alpha_3) E_2}{\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3}$$

————— (3)

Substituting the value of  $I_2$  in eqn. (1) we get,

$$I_1 = \frac{(\alpha_2 + \alpha_3) E_1}{\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3} - \frac{\alpha_3 E_2}{\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3} \quad (4)$$

Now, considering the circuit of figure (a) (b) we have the mesh equations,

$$E_1 = (\alpha_1 + \alpha_3) I_1' + \alpha_3 I_2' \quad (5)$$

$$0 = \alpha_3 I_1' + (\alpha_2 + \alpha_3) I_2' \quad (6)$$

Solving eqn. (5) and (6) we get,

$$I_2' = \frac{-\alpha_3 E_1}{[\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3]} \quad (7)$$

$$I_1' = \frac{(\alpha_2 + \alpha_3) E_1}{(\alpha_1 \alpha_2 + \alpha_2 \alpha_3 + \alpha_1 \alpha_3)} \quad (8)$$

Referring to circuit of figure (c) the mesh equations are,

$$0 = (\alpha_1 + \alpha_3) I_1'' + \alpha_3 I_2'' \quad (9)$$

$$E_2 = \alpha_3 I_1'' + (\alpha_2 + \alpha_3) I_2'' \quad (10)$$

Solving these equations, we have,

$$I_2'' = \frac{(z_1 + z_3) E_2}{z_1 z_2 + z_2 z_3 + z_1 z_3} \quad \text{--- (11)}$$

$$I_1'' = \frac{-z_3 E_2}{z_1 z_2 + z_2 z_3 + z_1 z_3} \quad \text{--- (12)}$$

From equation (3), (4), (7), (8), (11) and (12) we get,

$$I_1 = I_1' + I_1'' \quad \text{and}$$

$$I_2 = I_2' + I_2''$$

This proves the theorem.

